

OBJECTIVE TYPE QUESTIONS FOR PRACTICAL EXAMINATION
Subject: Fundamental of Electrical Engg. (EE-111)

1. Resistance is measured in
 - A. henries
 - B. ohms
 - C. hertz
 - D. watts

2. Which of the following is not an electrical quantity?
 - A. voltage
 - B. current
 - C. distance
 - D. power

3. Voltage is measured in
 - A. volts
 - B. farads
 - C. watts
 - D. ohms

4. Current is measured in
 - A. watts
 - B. volts
 - C. henries
 - D. amperes

5. The formula to find I when the values of V and R are known is
 - A. $I = VR$
 - B. $I = R/V$
 - C. $V = IR$
 - D. $I = V/R$

6. When there is 12 mA of current through a 1.2 k Ω resistor, the voltage across the resistor is
 - A. 14.4 V
 - B. 1.4 V

C. 100 V

D. 10 V

7. When a fourth resistor is connected in series with three resistors, the total resistance

A. increases by one-fourth

B. increases

C. decreases

D. remains the same

8. Two 6 V batteries are connected series aiding across two $1.2 \text{ k}\Omega$ resistors in series. Current through each resistor is


A. 5 mA

B. 10 mA

C. 0 A

D. 2.5 mA

9. Find the node voltage V_A .

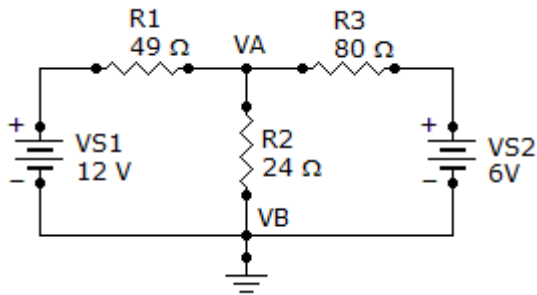


A. 6 V

B. 12 V

C. 4.25 V

D. 3 V

10. What is the current through R_2 ?

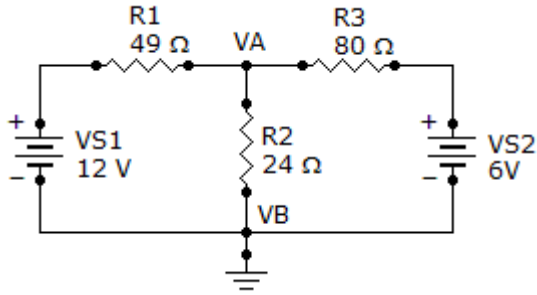

- A. 177 mA
 - B. 250 mA
 - C. 500 mA
 - D. 125 mA
11. The branch current method uses
- A. Kirchhoff's voltage and current laws
 - B. Thevenin's theorem and Ohm's law
 - C. Kirchhoff's current law and Ohm's law
 - D. the superposition theorem and Thevenin's theorem
12. If the rms voltage drop across a 15 k Ω resistor is 16 V, the peak current through the resistor is
- A. 15 mA
 - B. 1.5 mA
 - C. 10 mA
 - D. 1 mA
13. How many degrees are there in $\pi/3$ rad?
- A. 6°
 - B. 60°
 - C. 180°
 - D. 27°
14. The average value of a 12 V peak sine wave over one complete cycle is
- A. 0 V
 - B. 1.27 V
 - C. 7.64 V
 - D. 6.37 V
15. A phasor represents

- A. the magnitude and a quantity direction
- B. the width of a quantity
- C. the phase angle
- D. the magnitude of a quantity

16. A 2 mH, a 3.3 mH, and a 0.2 mH inductor are connected in series. The total inductance is

- A. 55 mH
- B. less than 0.2 mH
- C. less than 5.5 mH
- D. 5.5 mH

17. A sine wave voltage is applied across an inductor. When the frequency of the voltage is decreased, the current

- A. is increased
- B. is decreased
- C. does not change
- D. momentarily goes to zero

18. When the current through an inductor decreases, the amount of energy stored in the electromagnetic field

- A. increases
- B. decreases
- C. remains the same
- D. doubles

19. In a series RC circuit, $12\text{ V}_{(\text{rms})}$ is measured across the resistor and $15\text{ V}_{(\text{rms})}$ is measured across the capacitor. The rms source voltage is

- A. 3 V
- B. 27 V
- C. 19.2 V
- D. 1.9 V

20. A $10\ \Omega$ resistor, a 90 mH coil, and a $0.015\ \mu\text{F}$ capacitor are in series across an ac source. The impedance magnitude at 1,200 Hz below f_r is

- A. 1,616 Ω
- B. 161 Ω
- C. 3,387 Ω
- D. 1,771 Ω

21. The impedance at the resonant frequency of a series RLC circuit with $L = 20$ mH, $C = 0.02$ μ F, and $R_W = 90$ Ω is

- A. 0 Ω
- B. 90 Ω
- C. 20 k Ω
- D. 40 k Ω

22. A certain series RLC circuit with a 200 Hz, 15 V ac source has the following values: $R = 12$ Ω , $C = 80$ μ F, and $L = 10$ mH. The total impedance, expressed in polar form, is

- A. $12.28 \angle 12.34^\circ$ Ω
- B. $12.57 \angle 12.34^\circ$ Ω
- C. $9.95 \angle 12.34^\circ$ Ω
- D. $12.62 \angle 12.34^\circ$ Ω

23. The two basic components of a Thevenin equivalent ac circuit are

- A. the equivalent voltage source and the equivalent series impedance
- B. the equivalent voltage source and the equivalent series resistance
- C. the equivalent voltage source and the equivalent parallel impedance
- D. the equivalent voltage source and the equivalent parallel resistance

24. In applying the superposition theorem,

- A. the sources are considered one at a time with all others replaced by their internal impedance
- B. all sources are considered independently
- C. all sources are considered simultaneously
- D. the sources are considered one at a time with all others replaced by their internal resistance

25. In a three-phase system, the voltages are separated by

- A. 45°
- B. 90°
- C. 120°
- D. 180°

26. In a certain three-wire Y-connected generator, the phase voltages are 2 kV. The magnitudes of the line voltages are

- A. 2,000 V

B. 6,000 V

C. 666 V

D. 3,464 V

27. In a Y-connected circuit, between each line voltage and the nearest phase voltage, there is a phase angle of

A. 0°

B. 30°

C. 60°

D. 120°

28. The unit of electrical charge is the

A. volt

B. ampere

C. joule

D. coulomb

29. A multimeter measures


A. current

B. voltage

C. resistance

D. current, voltage, and resistance

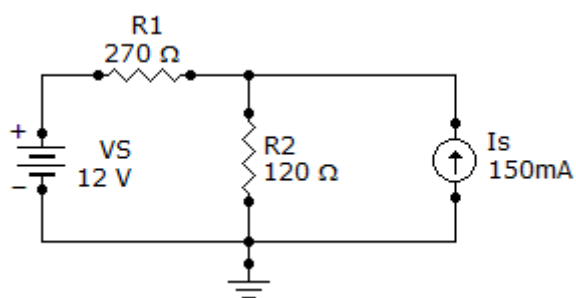30. Find the current through R_2 of the given circuit.



A. 30.7 mA

B. 104 mA

C. 74 mA

D. 134 mA

31. The induced voltage across a coil with 250 turns that is located in a magnetic field that is changing at a rate of 8 Wb/s is

- A. 1,000 V
- B. 2,000 V
- C. 31.25 V
- D. 3,125 V

32. What is the flux density when the flux is $5.5 \mu\text{Wb}$ and the cross-sectional area is $6 \times 10^{-3} \text{m}^2$?

- A. $91.7 \mu\text{T}$
- B. $917 \mu\text{T}$
- C. 91 T
- D. 9.7 T

33. The unit for reluctance is

- A. tesla
- B. At/Wb
- C. At/m
- D. Wb

34. The unit for permeability is

- A. $\text{Wb}/\text{At} \times \text{m}$
- B. At/m
- C. At/Wb
- D. Wb

35. The ability of a material to remain magnetized after removal of the magnetizing force is known as

- A. permeability
- B. reluctance
- C. hysteresis
- D. retentivity

36. The direction of a magnetic field within a magnet is

- A. from south to north
- B. from north to south
- C. back to front
- D. front to back

37. The voltage induced across a certain coil is 200 mV. A 120Ω resistor is connected to the

coil terminals. The induced current is

- A. 1.7 mA
- B. 16 mA
- C. 12 mA
- D. 120 mA

38. A certain transformer has 400 turns in the primary winding and 2,000 turns in the secondary winding. The turns ratio is

- A. 0.2
- B. 0.4
- C. 5
- D. 25

39. The mutual inductance when $k = 0.65$, $L_1 = 2 \mu\text{H}$, and $L_2 = 5 \mu\text{H}$ is

- A. 2 mH
- B. $2 \mu\text{H}$
- C. $4 \mu\text{H}$
- D. $8 \mu\text{H}$

40. A transformer

- A. changes ac to dc
- B. changes dc to ac
- C. steps up or down dc voltages
- D. steps up or down ac voltages

41. When a 6 V battery is connected across the primary of a transformer with a turns ratio of 8, the secondary voltage is

- A. 0 V
- B. 6 V
- C. 48 V
- D. 0.75 V

42. A $1.5 \text{ k}\Omega$ resistor and a coil with a $2.2 \text{ k}\Omega$ inductive reactance are in series across an 18 V ac source. The power factor is

- A. 564
- B. 0.564
- C. 6.76

D. 55.7

43. When the frequency is decreased, the impedance of a parallel RL circuit

A. increases

B. decreases

C. remains constant

D. is not a factor

44. If a load is purely inductive and the reactive power is 12 VAR, the apparent power is

A. 0 VA

B. 12 VA

C. 6 VA

D. 24 VA

45. When converting 7,000 nA to microamperes, the result is


A. 0.007 μA

B. 0.7 μA

C. 700 μA

D. 7 μA

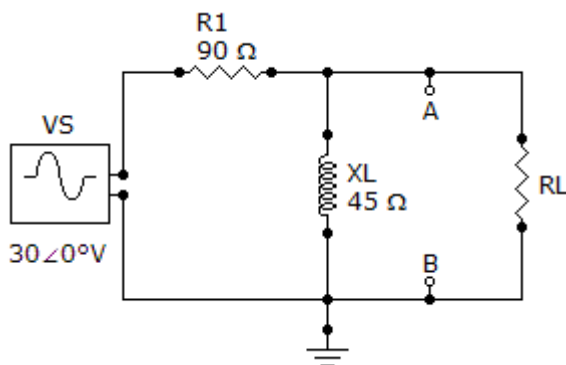46. Determine V_{TH} when R_1 is 180Ω and X_L is 90Ω .



A. $135 \angle 63.4^\circ \text{V}$

B. $13.5 \angle 63.4^\circ \text{V}$

C. $12.2 \angle 0^\circ \text{V}$

D. $122 \angle 0^\circ \text{V}$

47. If two currents are in the same direction at any instant of time in a given branch of a circuit, the net current at that instant
- A. is zero
 - B. is the sum of the two currents
 - C. is the difference between the two currents
 - D. cannot be determined
48. Three $10\text{ k}\Omega$ resistors are connected in series. A $20\text{ k}\Omega$ resistor is connected in parallel across one of the $10\text{ k}\Omega$ resistors. The voltage source is 24 V . The total current in the circuit is
- A. $900\ \mu\text{A}$
 - B. 9 mA
 - C. 90 mA
 - D. $800\ \mu\text{A}$
49. An 18 V source has an internal resistance of $70\ \Omega$. If a load resistance of $33\ \Omega$ is connected to the voltage source, the load power, P_L , is
- A. 0 W
 - B. 1 W
 - C. 175 mW
 - D. 18 mW
50. An electric heater draws 3.5 A from a 110 V source. The resistance of the heating element is approximately
- A. $385\ \Omega$
 - B. $38.5\ \Omega$
 - C. $3.1\ \Omega$
 - D. $31\ \Omega$

Answer Keys

S.No.	Ans	S.No.	Ans
1	B	26	D
2	C	27	C
3	A	28	D
4	D	29	D
5	C	30	D
6	A	31	B
7	B	32	B
8	A	33	B
9	C	34	A
10	A	35	D
11	A	36	A
12	B	37	A
13	B	38	C
14	A	39	B
15	A	40	D
16	D	41	A
17	A	42	B
18	B	43	B
19	C	44	B
20	A	45	D
21	B	46	B
22	A	47	B
23	A	48	A
24	A	49	B
25	C	50	D